



Introduction to Digital Design

Week 7: Clock, Latches, and Flip-Flops

Yao Zheng
University of Hawai'i at Mānoa
Department of Electrical and Computer Engineering

1

Overview


- Sequential circuit
 - Output depends not just on present inputs but on past sequence of inputs.
- SR Latch
 - Feedback circuit for bit storage.
 - Race condition and level-sensitive latch.
- D Latch and D Flip-Flop
 - D Latch: inserted inverter ensures R always opposite of S
 - D Flip-Flop: bit storage that stores on clock edge.
- Clock signal
 - Flip-flop to generates periodic pulsing signal.
- Basic register

2

Introduction

- Sequential circuit
 - Output depends not just on present inputs (as in combinational circuit), but on past sequence of inputs
 - Stores bits, also known as having "state"
 - Simple example: a circuit that counts up in binary
- This week we will:
 - Design a new building block, a **flip-flop**, to store one bit
 - Combine flip-flops to build multi-bit storage – **register**
- Next week we will:
 - Describe sequential behavior with **finite state machines**
 - Convert a finite state machine to a **controller** – sequential circuit with a register and combinational logic

3.1

 


Note: Slides with animation are denoted with a small red "a" near the animated items

3

Storing One Bit – Flip-Flops

 Example Requiring Bit Storage

- Flight attendant call button
 - Press call: light turns on
 - Stays on** after button released
 - Press cancel: light turns off
 - Stays off after button released
 - Logic gate circuit to implement this?




Doesn't work. $Q=1$ when $Call=1$, but doesn't stay 1 when $Call$ returns to 0
Need some form of "feedback" in the circuit

3.2

4

First attempt at Bit Storage

 - Need some sort of feedback
 - Does circuit on the right do what we want?
 - No: Once Q becomes 1 (when $S=1$), Q stays 1 forever – no value of S can bring Q back to 0




5

5

Bit Storage Using an SR Latch

 - Does the circuit to the right, with cross-coupled NOR gates, do what we want?
 - Yes! How did someone come up with that circuit? Maybe just trial and error, a bit of insight...




6

6

 Example Using SR Latch for Bit Storage


- SR latch can serve as bit storage in previous example of flight-attendant call button
 - Call=1 : sets Q to 1
 - Q stays 1 even after Call=0
 - Cancel=1 : resets Q to 0
- But, there's a problem...




7

Problem with SR Latch

 - Problem
 - If $S=1$ and $R=1$ simultaneously, we don't know what value Q will take



 
Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which. Known as a *race condition*.



8

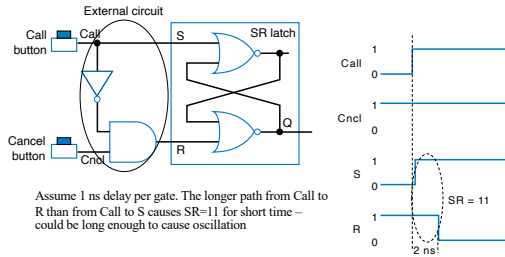Problem with SR Latch

- Designer might try to avoid problem using external circuit
 - Circuit should prevent SR from ever being 11
 - But 11 can occur due to different path delays




Assume 1 ns delay per gate. The longer path from Call to R than from Call to S causes $SR=11$ for short time – could be long enough to cause oscillation

9

 Problem with SR Latch

- Glitch can also cause undesired set or reset




Suppose this wire has 4 ns delay

$SR = 01$
(undesired glitch)

10

Solution: Level-Sensitive SR Latch

 - Add enable input "C"
- Only let S and R change when $C=0$
 - Ensure circuit in front of SR never sets $SR=11$, except briefly due to path delays
 - Set $C=1$ after time for S and R to be stable
 - When C becomes 1, the stable S and R value passes through the two AND gates to the SR latch's S1 R1 inputs.




Glitch on R (or S) doesn't affect R1 (or S1)

11

Level-Sensitive D Latch

 - SR latch requires careful design to ensure $SR=11$ never occurs
- D latch relieves designer of that burden
 - Inserted inverter ensures R always opposite of S



D latch symbol


12

11

12

 Problem with Level-Sensitive D Latch


- D latch still has problem (as does SR latch)
 - When $C=1$, through how many latches will a signal travel?
 - Depends on how long $C=1$
 - Clk_A – signal may travel through multiple latches
 - Clk_B – signal may travel through fewer latches



13

13

Problem with Level-Sensitive D Latch

 

14


14

D Flip-Flop

Can we design bit storage that only stores a value on the rising edge of a clock signal?

rising edges
clk

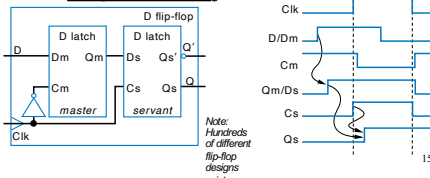- Flip-flop:** Bit storage that stores on clock edge
 - One design – master-servant
 - $\text{Clk} = 0$ – master enabled, loads D, appears at Qm. Servant disabled.
 - $\text{Clk} = 1$ – Master disabled, Qm stays same. Servant latch enabled, loads Qm, appears at Qs.
 - Thus, value at D (and hence at Qm) when Clk changes from 0 to 1 gets stored into servant




15

15

D Flip-Flop

 
- Solves problem of not knowing through how many latches a signal travels when $C=1$
 - In figure below, signal travels through exactly one flip-flop, for Clk_A or Clk_B
 - Why? Because on rising edge of Clk, all four flip-flops are loaded simultaneously – then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is 1.



16

16

D Flip-Flop

 


17

17

D Latch vs. D Flip-Flop

 - Latch is level-sensitive
 - Stores D when $C=1$
- Flip-flop is edge triggered
 - Stores D when C changes from 0 to 1
- Saying “level-sensitive latch” or “edge-triggered flip-flop” is redundant
- Comparing behavior of latch and flip-flop:



18

18

Summary

- Sequential circuit
 - Output depends not just on present inputs but on past sequence of inputs.
- SR Latch
 - Feedback circuit for bit storage.
 - Race condition and level-sensitive latch.
- D Latch and D Flip-Flop
 - D Latch: inserted inverter ensures R always opposite of S
 - D Flip-Flop: bit storage that stores on clock edge.
- Clock signal
 - Flip-flop to generates periodic pulsing signal.
- Basic register

25

25