



Introduction to Digital Design

Week 15: Programmable Processors and HDL

Yao Zheng
University of Hawai'i at Mānoa
Department of Electrical and Computer Engineering

1

Overview


- Programmable processors are widely used
 - Easy availability, short design time
- Basic architecture
 - Datapath with register file and ALU
 - Control unit with PC, IR, and controller
 - Memories for instructions and data
 - Control unit fetches, decodes, and executes
- Three-instruction processor with machine-level programs
 - Extended to six instructions
 - Real processors have dozens or hundreds of instructions
 - Extended to access external pins
 - Modern processors are far more sophisticated
- Hardware Description Languages (HDLs)
 - VHDL, Verilog, and SystemC are popular
 - Introduced languages mainly through examples

2

Programmable Processor

 8.1

- Programmable (general-purpose) processor
 - Mass-produced, then programmed to implement different processing tasks
 - Well-known common programmable processors: Pentium, Sparc, PowerPC
 - Lesser-known but still common: ARM, MIPS, 8051, PIC, AVR
 - Low-cost embedded processors found in cell phones, blinking shoes, etc.
 - Instructive to design a very simple programmable processor
 - Real processors can be much more complex



3-tap FIR filter single-purpose processor General-purpose processor


Note: Slides with animation are denoted with a small red "a" near the animated items.

3

Basic Architecture

 8.2

- Processing generally consists of:
 - Loading some data
 - Transforming that data
 - Storing that data
- **Basic datapath:** Useful circuit in a programmable processor
 - Can read/write data memory, where main data exists
 - Has register file to hold data locally
 - Has ALU to transform local data




Datapath

4

Basic Datapath Operations

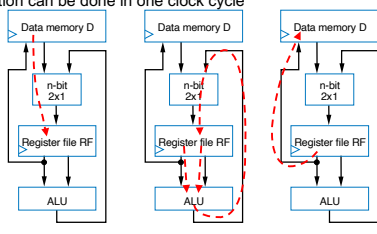- Load operation: Load data from data memory to RF
- ALU operation: Transforms data by passing one or two RF register values through ALU, performing operation (ADD, SUB, AND, OR, etc.), and writing back into RF.
- Store operation: Stores RF register value back into data memory
- Each operation can be done in one clock cycle




Load operation ALU operation Store operation

5

Basic Datapath Operations

- **Q:** Which are valid *single-cycle operations* for given datapath?
 - Move D[1] to RF[1] (i.e., $RF[1] = D[1]$)
 - **A:** YES – That's a load operation
 - Store RF[1] to D[9] and store RF[2] to D[10]
 - **A:** NO – Requires two separate store operations
 - Add D[0] plus D[1], store result in D[9]
 - **A:** NO – ALU operation (ADD) only works with RF. Requires two load operations (e.g., $RF[0]=D[0]$; $RF[1]=D[1]$), an ALU operation (e.g., $RF[2]=RF[0]+RF[1]$), and a store operation (e.g., $D[9]=RF[2]$)

 

Load operation ALU operation Store operation


6

Basic Architecture – Control Unit

- $D[9] = D[0] + D[1]$ – requires a sequence of four datapath operations:

```
0. RF[0] = D[0]
1. RF[1] = D[1]
2. RF[2] = RF[0] + RF[1]
3. D[9] = RF[2]
```


- Each operation is an *instruction*
 - Sequence of instructions – *program*
 - Looks cumbersome, but that's the world of programmable processors – Decomposing desired computations into processor-supported operations
 - Store program in *Instruction memory*
 - *Control unit* reads each instruction and executes it on the datapath
 - PC: Program counter – address of current instruction
 - IR: Instruction register – current instruction

 

7

7


Machine Model Summary

 

8

8


Machine Model Summary

 

9

9


Machine Model Summary

 

10

Basic Architecture – Control Unit

 - To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath




11

11

Basic Architecture – Control Unit

 - To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath




12

12

Basic Architecture – Control Unit

 
- To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath



13

Basic Architecture – Control Unit

 - To carry out *each instruction*, the control unit must:
 - Fetch – Read instruction from inst. mem.
 - Decode – Determine the operation and operands of the instruction
 - Execute – Carry out the instruction's operation using the datapath




14

Basic Architecture – Control Unit

To summarize, the control unit processes each instruction in three stages:

- first *fetching* the instruction by loading the current instruction into *IR* and incrementing the *PC* for the next fetch,
- next *decoding* the instruction to determine its operation, and
- finally *executing* the operation by setting the appropriate control lines for the datapath, if applicable. If the operation is a datapath operation, the operation may be one of three possible types:
 - loading a data memory location into a register file location,
 - transforming data using an *ALU* operation on register file locations and writing results back to a register file location, or
 - storing a register file location into a data memory location.

 

15

Creating a Sequence of Instructions

- Q:** Create sequence of instructions to compute $D[3] = D[0] + D[1] + D[2]$ on earlier-introduced processor
- A1:** One possible sequence
 - First load data memory locations into register file
 - $R[3] = D[0]$
 - $R[4] = D[1]$
 - $R[2] = D[2]$
 - Next, perform the additions
 - $R[1] = R[3] + R[4]$
 - $R[1] = R[1] + R[2]$
 - Finally, store result
 - $D[3] = R[1]$
- A2:** Alternative sequence
 - First load $D[0]$ and $D[1]$ and add them
 - $R[1] = D[0]$
 - $R[2] = D[1]$
 - $R[1] = R[1] + R[2]$
 - Next, load $D[2]$ and add
 - $R[2] = D[2]$
 - $R[1] = R[1] + R[2]$
 - Finally, store result
 - $D[3] = R[1]$

16


Number of Cycles

- Q:** How many cycles are needed to execute six instructions using the earlier-described processor?
- A:** Each instruction requires 3 cycles – 1 to fetch, 1 to decode, and 1 to execute
 - Thus, $6 \text{ instr} * 3 \text{ cycles/instr} = 18 \text{ cycles}$

17


Three-Instruction Programmable Processor

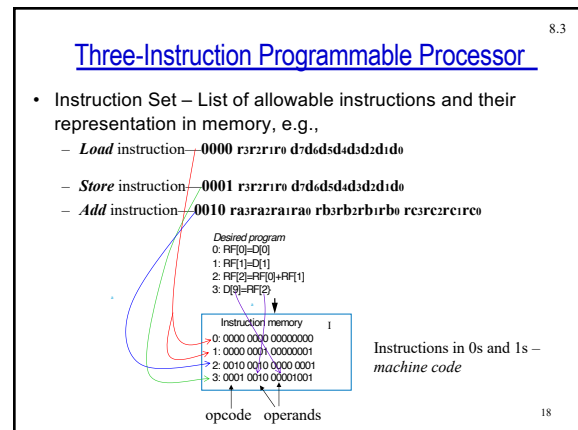- Instruction Set – List of allowable instructions and their representation in memory, e.g.,
 - Load instruction – 0000 r3r2r1r0 d7d6d5d4d3d2d1d0
 - Store instruction – 0001 r3r2r1r0 d7d6d5d4d3d2d1d0
 - Add instruction – 0010 ra3ra2ra1ra0 rb3rb2rb1rb0 rc3rc2rc1rc0



18

Program for Three-Instruction Processor

 

19

Program for Three-Instruction Processor

- Another example program in machine code
 - Compute $D[5] = D[5] + D[6] + D[7]$

```

0: 0000 0000 00000101 // RF[0] = D[5]
1: 0000 0001 00000110 // RF[1] = D[6]
2: 0000 0010 00000111 // RF[2] = D[7]
3: 0010 0000 0000 0001 // RF[0] = RF[0] + RF[1]
   // which is D[5]+D[6]
4: 0010 0000 0000 0010 // RF[0] = RF[0] + RF[2]
   // now D[5]+D[6]+D[7]
5: 0001 0000 00000101 // D[5] = RF[0]

```

-Load instruction—0000 rrrrrr dddddddddd
-Store instruction—0001 rrrrrr dddddddddd
-Add instruction—0010 rrrrrrrrrr rrrrrrrrrr rrrrrrrrrr

20

Assembly Code

- Machine code (0s and 1s) hard to work with
- Assembly code – Uses mnemonics
 - Load instruction—MOV Ra, d**
 - specifies the operation $RF[a] = D[d]$. a must be 0, 1, ..., or 15—so $R0$ means $RF[0]$, $R1$ means $RF[1]$, etc. d must be 0, 1, ..., 255
 - Store instruction—MOV d, Ra**
 - specifies the operation $D[d] = RF[a]$
 - Add instruction—ADD Ra, Rb, Rc**
 - specifies the operation $RF[a] = RF[b] + RF[c]$


Desired program	0: 0000 0000 00000000	0: MOV R0, 0
1: $RF[1] = D[1]$	1: 0000 0001 00000001	1: MOV R1, 1
2: $RF[2] = RF[0] + RF[1]$	2: 0010 0010 0000 0001	2: ADD R2, R0, R1
3: $D[9] = RF[2]$	3: 0001 0010 00001001	3: MOV 9, R2

machine code assembly code

21

Control-Unit and Datapath for Three-Instruction Processor

 
- To design the processor, we can begin with a high-level state machine description of the processor's behavior



22

Control-Unit and Datapath for Three-Instruction Processor

 
- Create detailed connections among components



23

Control-Unit and Datapath for Three-Instruction Processor

 - Convert high-level state machine description of entire processor to FSM description of controller that uses datapath and other components to achieve same behavior



24

A Six-Instruction Programmable Processor

- Let's add three more instructions:
 - Load-constant** instruction—0011 r3r2r1r0 c7c6c5c4c3c2c1c0
 - MOV Ra, #c—specifies the operation $RF[a] = c$
 - Subtract** instruction—0100 r3r2r1r0 r3r2r1r0 r3r2r1r0 r3r2r1r0
 - SUB Ra, Rb, Rc—specifies the operation $RF[a] = RF[b] - RF[c]$
 - Jump-if-zero** instruction—0101 r3r2r1r0 r3r2r1r0 0706050403020100
 - JMPZ Ra, offset—specifies the operation $PC = PC + offset$ if $RF[a]$ is 0

TABLE 8.1 Six-instruction instruction set.

Instruction	Meaning
MOV Ra, d	$RF[a] = D[d]$
MOV d, Ra	$D[d] = RF[a]$
ADD Ra, Rb, Rc	$RF[a] = RF[b] + RF[c]$
MOV Ra, #C	$RF[a] = C$
SUB Ra, Rb, Rc	$RF[a] = RF[b] - RF[c]$
JMPZ Ra, offset	$PC = PC + offset$ if $RF[a] = 0$

TABLE 8.2 Instruction opcodes.

Instruction	Opcodes
MOV Ra, d	0000
MOV d, Ra	0001
ADD Ra, Rb, Rc	0010
MOV Ra, #C	0011
SUB Ra, Rb, Rc	0100
JMPZ Ra, offset	0101

25


Extending the Control-Unit and Datapath

- The **load-constant** instruction requires that the register file be able to load data from $IR[7..0]$, in addition to data from data memory or the ALU output. Thus, we widen the register file's multiplexer from 2x1 to 3x1, add another mux control signal, and also create a new signal coming from the controller labeled RF_W_data , which will connect with $IR[7..0]$.

- The **subtract** instruction requires that we use an ALU capable of subtraction, so we add another ALU control signal.


- The **jump-if-zero** instruction requires that we be able to detect if a register is zero, and that we be able to add $IR[7..0]$ to the PC.
 - We insert a datapath component to detect if the register file's Rp read port is all zeros (that component would just be a NOR gate).

 - We also upgrade the PC register so it can be loaded with PC plus $IR[7..0]$. The adder used for this also subtracts 1 from the sum, to compensate for the fact that the **Fetch** state already added 1 to the PC .



26

 Controller FSM for the Six-Instruction Processor



27

Program for the Six-Instruction Processor

- Example program – Count number of non-zero words in D[4] and D[5]
 - Result will be either 0, 1, or 2
 - Put result in D[9]

```

MOV R0, #0; // initialize result to 0
MOV R1, #1; // constant 1 for incrementing result
MOV R2, 4; // get data memory location 4
JMPZ R2, lab1; // if zero, skip next instruction
ADD R0, R0, R1; // not zero, so increment result
lab1: MOV R2, 5; // get data memory location 5
JMPZ R2, lab2; // if zero, skip next instruction
ADD R0, R0, R1; // not zero, so increment result
lab2: MOV R0, R0; // store result in data memory location 9

```

(a)

(b)

Instruction	Opcodes
MOV Ra, d	0000
MOV d, Ra	0001
ADD Ra, Rb, Rc	0010
MOV Ra, #C	0011
SUB Ra, Rb, Rc	0100
JMPZ Ra, offset	0101

28

Further Extensions to the Programmable Processor


- Typical processor instruction set will contain dozens of data movement (e.g., loads, stores), ALU (e.g., add, sub), and flow-of-control (e.g., jump) instructions

- Extending the control-unit/datapath follows similarly to previously-shown extensions

- Input/output extensions


- Certain memory locations may actually be external pins

 - e.g., D[240] may represent 8-bit input I0, D[255] may represent 8-bit output P7



29

 Program using I/O Extensions – Recall Chpt 1 C-Program Example




30

Program Using Input/Output Extensions

Underlying assembly code for C expression `!0 && !1`.

```
0: MOV R0, 240 // move D[240], which is the value at pin I0, into R0
1: MOV R1, 241 // move D[241], which is that value at pin I1, into R1
2: NOT R1, R1 // compute !I1, assuming existence of a complement instruction
3: AND R0, R0, R1 // compute I0 && !I1, assuming an AND instruction
4: MOV 248, R0 // move result to D[248], which is pin P0
```
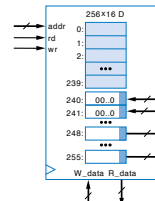
```
void main()
{
    while (1) {
        P0 = I0 && !I1;
        // F = a and !b,
    }
}
```



31



31

Hardware description language

- A drawing of a circuit, or *schematic*, contains graphical information about a design

- Such graphical information may not be useful for large designs

- Can use textual language instead

  


Note: Slides with animation are denoted with a small red "a" near the animated items

32

32

Textual Language – English

 - Can describe circuit using English text rather than using a drawing
 - Of course, English isn't a good language for a computer to read
 - Need a more precise, computer-oriented language



(b) We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:

- An inverter, which has a bit input x, and bit output $\bar{x}$.
- A 2-input OR gate, which has inputs x and y, and bit output F.
- A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits. The DoorOpener circuit internally consists of:

- An inverter named inv_1, whose input x connects to external input c, and whose output connects to n1.
- A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
- A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.

That's all.

33

33

Computer-Readable Textual Language for Describing Hardware Circuits: HDLs


- Hardware description language (HDL)
 - Intended to describe circuits textually, for a computer to read
 - Evolved starting in the 1970s and 1980s
- Popular languages today include:
 - VHDL – Defined in 1980s by U.S. military; Ada-like language
 - Verilog – Defined in 1980s by a company; C-like language
 - SystemC – Defined in 2000s by several companies; consists of libraries in C++

34

34

Combinational Logic Description using Hardware Description Languages^{9.2}

 - Structure**
 - Another word for "circuit"
 - An interconnection of components
 - Key use of HDLs is to describe structure



Note: The term "instantiate" will be used to indicate adding a new copy of a component to a circuit

The OR component



Three instances of the OR component




35

35

Describing Structure in VHDL

 - Entity – Defines new item's name & ports (inputs/outputs)
 - std_logic means bit type, defined in ieee library
- Architecture – Describes internals, which we named "Circuit"
 - Declares 3 previously-defined components
 - Declares internal signals
 - Note "-" comment
 - Instantiates and connects those components



We'll now describe a circuit whose name is DoorOpener. The external inputs are c, h and p, which are bits. The external output is f, which is a bit.

We assume you know the behavior of these components:

- An inverter, which has a bit input x, and bit output $\bar{x}$.
- A 2-input OR gate, which has inputs x and y, and bit output F.
- A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.

The DoorOpener circuit internally consists of:

- An inverter named inv_1, whose input x connects to external input c, and whose output connects to n1.
- A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
- A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.

That's all.

```
library ieee;
use ieee.std_logic_1164.all;
entity DoorOpener is
    port (
        c: in std_logic;
        h: in std_logic;
        p: in std_logic;
        f: out std_logic
    );
end entity;


architecture Circuit of DoorOpener is
    component Inv
        port (
            in: in std_logic;
            out: out std_logic
        );
    end component;
    component OR2
        port (
            in1: in std_logic;
            in2: in std_logic;
            out: out std_logic
        );
    end component;
    component AND2
        port (
            in1: in std_logic;
            in2: in std_logic;
            out: out std_logic
        );
    end component;
    signal n1, n2: std_logic; -- internal wires
begin
    inv1: Inv port map (a=c, b=n1);
    OR2_1: OR2 port map (a=h, b=p, c=n2);
    AND2_1: AND2 port map (a=n1, b=n2, c=f);
end architecture;
```

36

36

Describing Structure in Verilog

 
- Modules defined for Inv, OR2, and AND2 (details omitted)
 - Note "//" comment
- Module defined for DoorOpener
 - Lists inputs and outputs
 - Declares internal wires
 - Instantiates and connects three components



37

Describing Structure in SystemC

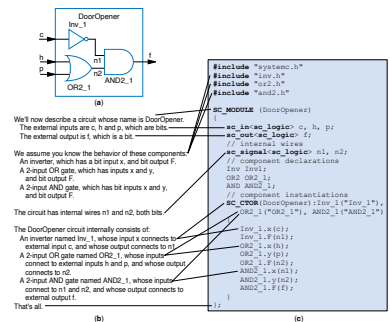- Module defined
 - Declares inputs and outputs
 - Declares internal wires
 - Note "//" comment
 - Declares three previously-defined components
 - Constructor function "CTOR"
 - Instantiates components
 - Connects components



38

Combinational Behavior

- Combinational behavior**
 - Description of desired behavior of combinational circuit without creating circuit itself
 - e.g., $F = c * (h + p)$ can be described as equation rather than circuit
 - HDLs support description of combinational behavior

39

Describing Combinational Behavior in VHDL

- Describing an OR gate's behavior
 - Entity defines input/output ports
 - Architecture
 - Process – Describes behavior
 - Process "sensitive" to x and y
 - Means behavior only executes when x changes or y changes
 - Behavior assigns a new value to output port F, computed using built-in operator "or"

```

library ieee;
use ieee.std_logic_1164.all;

entity OR2 is
  port (x, y: in std_logic;
        F: out std_logic);
end OR2;

architecture behavior of OR2 is
begin
  process (x, y)
  begin
    F <= x or y;
  end process;
end behavior;
  
```

40

Describing Combinational Behavior in VHDL

- Describing a custom function's behavior
 - Desired function: $f = c * (h + p)$
 - Entity defines input/output ports (not shown)
 - Architecture
 - Process
 - Sensitive to c, h, and p
 - Assigns a new value to output port f, computed using built-in operators "not", "and", and "or"

```

architecture beh of DoorOpener is
begin
  process(c, h, p)
  begin
    f <= not(c) and (h or p);
  end process;
end beh;
  
```

41

Describing Combinational Behavior in Verilog

- Describing an OR gate's behavior
 - Module declares input/output ports
 - Also indicates that F is "reg"
 - Means F stores value
 - By default, ports are wires, having no storage
 - "always" procedure executes statement block when change occurs on x or on y
 - "Sensitive" to x and y
 - Assigns value to F, computed using built-in OR operator "|"

```

module OR2(x, y, F);
  input x, y;
  output F;
  reg F;
  always @(x or y)
  begin
    F <= x | y;
  end
endmodule
  
```

42

Describing Combinational Behavior in Verilog

- Describing a custom function's behavior
 - Desired function: $f = c * (h + p)$
 - Module defines input/output ports
 - Output f defined as "reg"
 - "always" procedure sensitive to inputs
 - Assigns value to f , computed using built-in operators for NOT (~), AND (&), and OR (|)

```
module DoorOpener(c,h,p,f)
input c, h, p;
output f;
reg f;
always @(c or h or p)
begin
  f <= (~c) & (h | p);
end
endmodule
```

43

Describing Combinational Behavior in SystemC

- Describing an OR gate's behavior
 - Module declares input/output ports
 - Constructor (CTOR)
 - Indicates module described by a method (procedure) "comblogic"
 - Sensitive to x and y
 - Method "comblogic" assigns F a new value using built-in OR operator "|"
 - Reading input port done using .read() function defined for input port type; likewise, writing done using .write() function

```
#include "systemc.h"
SC_MODULE(OR2)
{
  sc_in<sc_logic> x, y;
  sc_out<sc_logic> F;
  SC_CTOR(OR2)
  {
    SC_METHOD(comblogic);
    sensitive << x << y;
  }
  void comblogic()
  {
    F.write(x.read() | y.read());
  }
};
```

44

Describing Combinational Behavior in SystemC


- Describing a custom function's behavior
 - Desired function: $f = c * (h + p)$
 - Module defines input/output ports
 - Constructor
 - Indicates module described by a method (procedure) "comblogic"
 - Sensitive to c , h , and p
 - "comblogic" method
 - Assigns value to f , computed using built-in operators for NOT (~), AND (&), and OR (|)

```
#include "systemc.h"
SC_MODULE(DoorOpener)
{
  sc_in<sc_logic> c, h, p;
  sc_out<sc_logic> f;
  SC_CTOR(DoorOpener)
  {
    SC_METHOD(comblogic);
    sensitive << c << h << p;
  }
  void comblogic()
  {
    f.write((~c.read()) & (h.read() | p.read()));
  }
};
```

45

Testbenches

 
- Testbench**
 - Assigns values to a system's inputs, check that system outputs correct values
 - A key use of HDLs is to simulate system to ensure design is correct



46

Testbench in VHDL

 - Entity
 - No inputs or outputs
- Architecture
 - Declares component to test, declares signals
 - Instantiates component, connects to signals
 - Process writes input signals, checks output signal
 - Waits a small amount of time after writing input signals
 - Checks for correct output value using "assert" statement




```
library ieee;
use ieee.std_logic_1164.all;

entity Testbench is
and Testbench
architecture behavior of Testbench is
  component DoorOpener
    port (
      c: in std_logic;
      h: in std_logic;
      p: in std_logic;
      f: out std_logic
    );
  end component;
  signal c, h, p, f: std_logic;
  begin
    DoorOpener1: DoorOpener port map (c,h,p,f);
  process
  begin
    -- case 0
    c <= '0'; h <= '0'; p <= '0';
    wait for 1 ns;
    assert (f='0') report "Case 0 failed";
    -- case 1
    c <= '0'; h <= '0'; p <= '1';
    wait for 1 ns;
    assert (f='1') report "Case 1 failed";
    -- (cases 2-6 omitted from figure)
    -- case 7
    c <= '1'; h <= '1'; p <= '1';
    wait for 1 ns;
    assert (f='0') report "Case 7 failed";
    wait -- process does not wake up again
  end process;
end behavior;
```

47

Testbench in Verilog

 - Module
 - Three register signals for inputs (values must be written and stored)
 - One wire signal for output (value is only read, need not be stored)
 - Instantiates component, connects to signals
 - "initial" procedure executed only once at beginning
 - Sets input values
 - Displays output value




```
module Testbench;
  reg c, h, p;
  wire f;
  DoorOpener DoorOpener1(c, h, p, f);
  initial
  begin
    // case 0
    c <= 0; h <= 0; p <= 0;
    #1 $display("f = %b", f);
    // case 1
    c <= 0; h <= 0; p <= 1;
    #1 $display("f = %b", f);
    // (cases 2-6 omitted from figure)
    // case 7
    c <= 1; h <= 1; p <= 1;
    #1 $display("f = %b", f);
  end
endmodule
```

48

Testbench in SystemC

 - Module
 - Testbench is its own module
 - Three outputs, one for each input of system to test
 - One input, for the one output of the system to test
 - Constructor defined as THREAD
 - Like MODULE, but allows use of "wait" to control timing
 - testbench procedure writes outputs, waits for small amount of time, checks for correct output
 - assert function prints error if condition is not true



```
#include "systemc.h"
SC_MODULE(Testbench)
{
    sc_out<sc_logic> c_t, h_t, p_t;
    sc_in<sc_logic> f_t;
    SC_CTOR(Testbench)
    {
        SC_THREAD(testbench_proc);
    }

    void testbench_proc()
    {
        // case 0
        c_t.write(SC_LOGIC_0);
        h_t.write(SC_LOGIC_0);
        p_t.write(SC_LOGIC_0);
        wait(1, SC_NS);
        assert(f_t.read() == SC_LOGIC_0);

        // case 1
        c_t.write(SC_LOGIC_0);
        h_t.write(SC_LOGIC_0);
        p_t.write(SC_LOGIC_1);
        wait(1, SC_NS);
        assert(f_t.read() == SC_LOGIC_1);

        // (cases 2-6 omitted from figure)
        // case 7
        c_t.write(SC_LOGIC_1);
        h_t.write(SC_LOGIC_1);
        p_t.write(SC_LOGIC_1);
        wait(1, SC_NS);
        assert(f_t.read() == SC_LOGIC_0);

        sc_stop();
    }
};
```

49

Sequential Logic Description using Hardware Description Languages ^{9.3}

- Will consider description of three sequential components
 - Registers
 - Oscillators
 - Controllers

50

Describing a 4-bit Register in VHDL

- Entity
 - 4 data inputs, 4 data outputs, and a clock input
 - Use std_logic_vector for 4-bit data
 - I: in std_logic_vector(3 downto 0)
 - I <= "1000" would assign I(3)=1, I(2)=0, I(1)=0, I(0)=0
- Architecture
 - Process sensitive to clock input
 - First statement detects if change on clock was a rising edge
 - If clock change was rising edge, sets output Q to input I
 - Ports are signals, and signals store values – thus, output retains new value until set to another value

```
library ieee;
use ieee.std_logic_1164.all;

entity Reg4 is
    port ( I: in std_logic_vector(3 downto 0);
          Q: out std_logic_vector(3 downto 0);
          clk: in std_logic );
end Reg4;

architecture behavior of Reg4 is
    process(clk)
    begin
        if (clk='1' and clk'event) then
            Q <= I;
        end if;
    end process;
end behavior;
```

51

Describing a 4-bit Register in Verilog

- Module
 - 4 data inputs, 4 data outputs, and a clock input
 - Define data inputs/outputs as vectors
 - input [3:0] I
 - I <= 4'b1000 assigns I[3]=1, I[2]=0, I[1]=0, I[0]=0
 - Output defined as register to store value
 - "always" procedure sensitive to positive (rising) edge of clock
 - Sets output Q to input I

```
module Reg4(I, Q, clk);
    input [3:0] I;
    input clk;
    output [3:0] Q;
    reg [3:0] Q;

    always @(posedge clk)
        Q <= I;
endmodule
```

52

Describing a 4-bit Register in SystemC

- Module
 - 4 data inputs, 4 data outputs, and a clock input
 - Define data inputs/outputs as vectors
 - sc_in<sc_lv<4> > I;
 - I <= "1000" assigns I[3]=1, I[2]=0, I[1]=0, I[0]=0
 - Constructor calls seq_logic method, sensitive to positive (rising) edge of clock
 - seq_logic writes output Q with input I
 - Output port is signal, and signal has storage, thus output retains value

```
#include "systemc.h"
SC_MODULE(Reg4)
{
    sc_in<sc_lv<4> > I;
    sc_out<sc_lv<4> > Q;
    sc_in<sc_logic> clk;

    SC_CTOR(Reg4)
    {
        SC_METHOD(seq_logic);
        sensitive_pos << clk;
    }

    void seq_logic()
    {
        Q.write(I.read());
    }
};
```

53

Describing an Oscillator in VHDL

- Entity
 - Defines clock output
- Architecture
 - Process
 - Has no sensitivity list, so executes non-stop as infinite loop
 - Sets clock to 0, waits 10 ns, sets clock to 1, waits 10 ns, repeats

```
library ieee;
use ieee.std_logic_1164.all;

entity Osc is
    port ( clk: out std_logic );
end Osc;

architecture behavior of Osc is
    process
    begin
        clk <= '0';
        wait for 10 ns;
        clk <= '1';
        wait for 10 ns;
    end process;
end behavior;
```

54

Describing an Oscillator in Verilog

- Module
 - Has one output, clk
 - Declare as "reg" to hold value
 - "always" procedure
 - Has no sensitivity list, so executes non-stop as infinite loop
 - Sets clock to 0, waits for 10 ns, sets clock to 1, waits for 10 ns, repeats

```
module Osc(clk);
  output clk;
  reg clk;

  always
  begin
    clk <= 0;
    #10;
    clk <= 1;
    #10;
  end
endmodule
```

55

55

Describing an Oscillator in SystemC

- Module
 - Has one output, clk
 - Constructor creates single thread
 - Thread consists of infinite loop
 - while (true) {
 - Sets clock to 0, waits 10 ns, sets clock to 1, waits 10 ns, repeats

```
#include "systemc.h"
SC_MODULE(Osc)
{
  sc_out<sc_logic> clk;


  SC_CTOR(Osc)
  {
    SC_THREAD(seq_logic);
  }

  void seq_logic()
  {
    while(true) {
      clk.write(SC_LOGIC_0);
      wait(10, SC_NS);
      clk.write(SC_LOGIC_1);
      wait(10, SC_NS);
    }
  }
};
```

56

56

Describing a Controller in VHDL

 

- FSM behavior captured using architecture with 2 processes
 - First process models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
- Note declaration of new type, statetype

```
library ieee;
use ieee.std_logic_1164.all;

entity LaserTimer is
  port (b: in std_logic;
        clk, rst: in std_logic);
end LaserTimer;


architecture behavior of LaserTimer is
  type statetype is
    (S_Off, S_On1, S_On2, S_On3);
  signal currentstate, nextstate: statetype;
begin
  statereg: process(clk, rst)
  begin
    if (rst='1') then -- initial state
      currentstate <= S_Off;
    elsif (clk='1' and clk'event) then
      currentstate <= nextstate;
    end if;
  end process;

  comblogic: process (currentstate, b)
  begin
    case currentstate is
      when S_Off =>
        x <= '0'; -- laser off
        if (b='0') then
          nextstate <= S_Off;
        else
          nextstate <= S_On1;
        end if;
      when S_On1 =>
        x <= '1'; -- laser on
        nextstate <= S_On2;
      when S_On2 =>
        x <= '1'; -- laser still on
        nextstate <= S_On3;
      when S_On3 =>
        x <= '1'; -- laser still on
        nextstate <= S_Off;
    end case;
  end process;
end behavior;
```

57

57

Describing a Controller in Verilog

 

- FSM behavior captured using 2 "always" procedures
 - First procedure models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
- Note state register size must be explicit – 2 bits, reg [1:0] currentstate

```
module LaserTimer(b, x, clk, rst);
  input b, clk, rst;
  output y;
  reg y;


  parameter S_Off = 2'b00,
            S_On1 = 2'b01,
            S_On2 = 2'b10,
            S_On3 = 2'b11;

  reg [1:0] currentstate;
  reg [1:0] nextstate;
  // state register procedure
  always @(posedge clk or negedge rst)
  begin
    if (rst==1) // initial state
      currentstate <= S_Off;
    else
      currentstate <= nextstate;
    end
  end
  // combinational logic procedure
  always @(currentstate or b)
  begin
    case (currentstate)
      S_Off: begin
        x <= 0; // laser off
        if (b==0)
          nextstate <= S_Off;
        else
          nextstate <= S_On1;
        end
      S_On1: begin
        x <= 1; // laser on
        nextstate <= S_On2;
        end
      S_On2: begin
        x <= 1; // laser still on
        nextstate <= S_On3;
        end
      S_On3: begin
        x <= 1; // laser still on
        nextstate <= S_Off;
        end
    endcase
  end
endmodule
```

58

58

Describing a Controller in SystemC

 

- FSM behavior captured using 2 methods
 - First method models state register
 - Asynchronous reset sets state to "S_Off"
 - Rising clock edge sets currentstate to nextstate
 - Second process models combinational logic
 - Sensitive to currentstate and FSM inputs
 - Sets FSM outputs based on currentstate
 - Sets nextstate based on currentstate and present FSM input values
- Note use of new type, statetype

```
#include "systemc.h"
enum statetype { S_Off, S_On1, S_On2, S_On3 };
SC_MODULE(LaserTimer)
{
  sc_in<sc_logic> x;
  sc_out<sc_logic> y;
  sc_signal<statetype> currentstate, nextstate;

  SC_CTOR(LaserTimer)
  {
    SC_METHOD(statereg);
    sensitive_pos <= rst << clk;
    SC_METHOD(comblogic);
    sensitive << currentstate << b;
  }

  void statereg() {
    if (rst.read() == SC_LOGIC_1)
      currentstate = S_Off; // initial state
    else
      currentstate = nextstate;
  }

  void comblogic() {
    switch (currentstate) {
      case S_Off:
        x.write(SC_LOGIC_0); // laser off
        if (!b.read() == SC_LOGIC_1)
          nextstate = S_Off;
        else
          nextstate = S_On1;
        break;
      case S_On1:
        x.write(SC_LOGIC_1); // laser on
        nextstate = S_On2;
        break;
      case S_On2:
        x.write(SC_LOGIC_1); // laser still on
        nextstate = S_On3;
        break;
      case S_On3:
        x.write(SC_LOGIC_1); // laser still on
        nextstate = S_Off;
        break;
    }
  }
};
```

59

59

Datapath Component Description using Hardware Description Languages

9.4


- Will consider description of three datapath components
 - Full-adders
 - Carry-ripple adders
 - Up-counter

60

60

Describing a Full-Adder in VHDL

 
- Entity
 - Declares inputs/outputs
- Architecture
 - Described behaviorally (could have been described structurally)
 - Process sensitive to inputs
 - Computes expressions, sets outputs



61

Describing a Full-Adder in Verilog

 
- Module
 - Declares inputs/outputs
 - Described behaviorally (could have been described structurally)
 - "always" procedure
 - Sensitive to inputs
 - Computes expressions, sets outputs



62

Describing a Full-Adder in SystemC

 
- Module
 - Declares inputs/outputs
 - Described behaviorally (could have been described structurally)
 - comblogic method
 - Computes expressions, sets outputs



63

Describing a Carry-Ripple Adder in VHDL

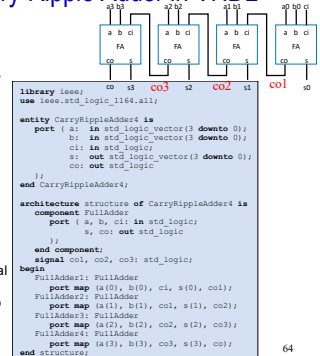
- Entity
 - Declares inputs/outputs
 - Uses std_logic_vector for 4-bit inputs/outputs
- Architecture
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Declares full-adder component, instantiates four full-adders, connects
 - Note use of three internal signals for connecting carry-out of one stage to carry-in of next stage



64

Describing a Carry-Ripple Adder in Verilog

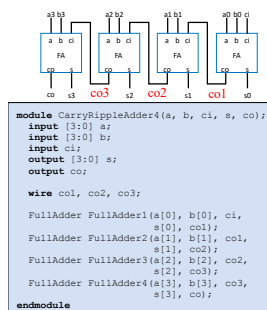
- Module
 - Declares inputs/outputs
 - Uses vectors for 4-bit inputs/outputs
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Instantiates four full-adders, connects
 - Note use of three internal wires for connecting carry-out of one stage to carry-in of next stage



65


Describing a Carry-Ripple Adder in SystemC

 - Module
 - Declares inputs/outputs
 - Uses vectors for 4-bit inputs/outputs
 - Described structurally by composing four full-adders (could have been described behaviorally instead)
 - Instantiates four full-adders, connects
 - Note use of three internal wires for connecting carry-out of one stage to carry-in of next stage



66

 Controller of Laser-Based Distance Measurer: Verilog



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-procedure FSM description approach

```

module LDM_Controller
  (clk, rst, B, S, L, Dreg_clk,
   Dreg_id, Dctr_clr, Dctr_id);
  input [1:0] rst, B, S;
  output Dreg_clk, Dreg_id;
  output Dctr_clr, Dctr_id;
  reg [1:0] State;
  reg [1:0] Dreg_id;
  reg [1:0] Dctr_id;
  parameter S0 = 3'b000,
            S1 = 3'b001,
            S2 = 3'b010,
            S3 = 3'b011,
            S4 = 3'b100;
  reg [1:0] Dreg_id;
  reg [1:0] Dctr_id;
  always @(posedge rst or posedge clk)
  begin
    State <= S0; // initial state
  end
  always @(clk)
  begin
    State <= StateNext;
  end
endmodule

```

```


always @(State or B or S)
begin
  Dreg_id <= 0;
  Dctr_id <= 0;
  Dctr_clr <= 0;
  Dctr_id <= 0;
  case (State)
    S0: // laser off
      Dreg_id <= 1; // clear Dreg
      StateNext <= S1;
    S1: // laser on
      Dctr_clr <= 1; // clear count
      if (B==1)
        StateNext <= S2;
      else
        StateNext <= S1;
    S2: // laser on
      L <= 0; // laser on
      Dctr_id <= 1; // count up
      if (S==1)
        StateNext <= S4;
      else
        StateNext <= S3;
    S3: // laser off
      Dreg_id <= 1; // load Dreg
      Dctr_id <= 0; // stop count
      StateNext <= S1;
    S4: // laser off
      Dreg_id <= 1; // load Dreg
      Dctr_id <= 0; // stop count
      StateNext <= S1;
  end
endcase
end
endmodule

```

79

Controller and DP of Laser-Based Distance Measurer: SystemC

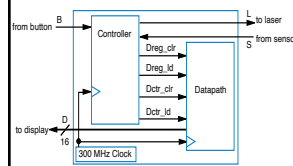- At highest level, just connection of controller and datapath components



```

#include "systemc.h"
#include "LDM_Controller.h"
#include "LDM_Datapath.h"

SC_MODULE(LaserDistMeasurer)
{
  sc_in<sc_logic> clk, rst;
  sc_in<sc_logic> B, S;
  sc_out<sc_logic> L;
  sc_out<sc_uint16> D;

  sc_signal<sc_logic> Dreg_clk, Dreg_id;
  sc_signal<sc_logic> Dctr_clr, Dctr_id;


  LDM_Controller LDM_Controller_1;
  LDM_Datapath LDM_Datapath_1;

  SC_CTOR(LaserDistMeasurer) :
    LDM_Controller_1("LDM_Controller_1"),
    LDM_Datapath_1("LDM_Datapath_1")
  {
    LDM_Controller_1.clk(clk);
    LDM_Controller_1.rst(rst);
    LDM_Controller_1.B(B);
    LDM_Controller_1.S(S);
    LDM_Controller_1.Dreg_clk(Dreg_clk);
    LDM_Controller_1.Dreg_id(Dreg_id);
    LDM_Controller_1.Dctr_clr(Dctr_clr);
    LDM_Controller_1.Dctr_id(Dctr_id);
    LDM_Datapath_1.clk(clk);
    LDM_Datapath_1.Dreg_clk(Dreg_clk);
    LDM_Datapath_1.Dreg_id(Dreg_id);
    LDM_Datapath_1.Dctr_clr(Dctr_clr);
    LDM_Datapath_1.Dctr_id(Dctr_id);
    LDM_Datapath_1.D(D);
  }
}

```

80

 DP of Laser-Based Distance Measurer: SystemC



- Datapath just another connection of components
 - Assume adder, register, and shift-right components are already designed (similar to earlier-designed items)

```

#include "systemc.h"
#include "add16.h"
#include "shiftr16.h"

SC_MODULE(LDM_Datapath)
{
  sc_in<sc_logic> clk;
  sc_in<sc_logic> Dreg_id, Dctr_clr, Dctr_id;
  sc_out<sc_uint16> D;
  sc_signal<sc_uint16> tempC;
  sc_signal<sc_uint16> addC;
  sc_signal<sc_uint16> shiftrC;


  Add16 Add1;
  Shiftr16 Shiftr;
  Dreg reg16;

  SC_CTOR(LDM_Datapath) :
    Add1("Add1"),
    Shiftr("Shiftr"),
    reg16("reg16")
  {
    Add1.A1();
    Add1.A2(tempC);
    Add1.A3(addC);
    Shiftr.I1(tempC);
    Shiftr.I2(shiftrC);
    reg16.Dreg_id(Dreg_id);
    reg16.Dctr_clr(Dctr_clr);
    reg16.Dctr_id(Dctr_id);
    reg16.Dreg_clk(Dreg_clk);
    reg16.Dreg_id(Dreg_id);
    reg16.Dctr_clr(Dctr_clr);
    reg16.Dctr_id(Dctr_id);
  }
}

```

81

 Controller of Laser-Based Distance Measurer: SystemC



- FSM similar to high-level state machine
 - But high-level operations replaced by low-level datapath signals
 - Use two-procedure FSM description approach

```

#include "systemc.h"

enum statetype { S0, S1, S2, S3, S4 };

SC_MODULE(LDM_Controller)
{
  sc_in<sc_logic> clk, rst, B, S;
  sc_out<sc_logic> L;
  sc_out<sc_uint16> D;
  sc_signal<sc_logic> Dreg_clk, Dreg_id;
  sc_signal<sc_logic> Dctr_clr, Dctr_id;

  SC_CTOR(LDM_Controller) :
    sensitive<< State << B << S;
  {
    void statereg() {
      if (rst.read() == SC_LOGIC_1)
        State = S0; // initial state
      else
        State = StateNext;
    }
  }
}

```

```

void comblogic() {
  L.write(SC_LOGIC_0);
  Dreg_id.write(SC_LOGIC_0);
  Dctr_clr.write(SC_LOGIC_0);
  Dctr_id.write(SC_LOGIC_0);
  D.write(SC_UINT16_0);

  switch (State) {
    case S0:
      Dctr_clr.write(SC_LOGIC_1); // laser off
      Dreg_id.write(SC_LOGIC_1);
      StateNext = S1;
      break;
    case S1:
      Dctr_clr.write(SC_LOGIC_1); // laser on
      Dreg_id.write(SC_LOGIC_1);
      if (B.read() == SC_LOGIC_1)
        StateNext = S2;
      else
        StateNext = S1;
      break;
    case S2:
      L.write(SC_LOGIC_0); // laser off
      Dctr_id.write(SC_LOGIC_1);
      if (S.read() == SC_LOGIC_1)
        StateNext = S4;
      else
        StateNext = S3;
      break;
    case S3:
      Dreg_id.write(SC_LOGIC_1);
      Dctr_id.write(SC_LOGIC_0);
      StateNext = S1;
      break;
    case S4:
      Dreg_id.write(SC_LOGIC_1);
      Dctr_id.write(SC_LOGIC_0);
      StateNext = S1;
      break;
  }
}

```

82

Summary

- Programmable processors are widely used
 - Easy availability, short design time
- Basic architecture
 - Datapath with register file and ALU
 - Control unit with PC, IR, and controller
 - Memories for instructions and data
 - Control unit fetches, decodes, and executes
- Three-instruction processor with machine-level programs
 - Extended to six instructions
 - Real processors have dozens or hundreds of instructions
 - Extended to access external pins
 - Modern processors are far more sophisticated
- Hardware Description Languages (HDLs)
 - VHDL, Verilog, and SystemC are popular
 - Introduced languages mainly through examples

83

83